



Section 8.5

24. Determine $i(t)$ for $t > 0$ in the preceding circuit if both switches have been open for a very long time, switch 2 is closed at $t = 0$, and reopened at $t = 0.2$ s.
25. Determine $v(t)$ for $t > 0$ in the following circuit if the switch has been open for a very long time, is closed at $t = 0$, and reopened at $t = 0.1$ s.

