

EXERCISE 11.4 Write a truth table and a boolean expression that describes the operation of each of the digital circuits in Figure 11.28.

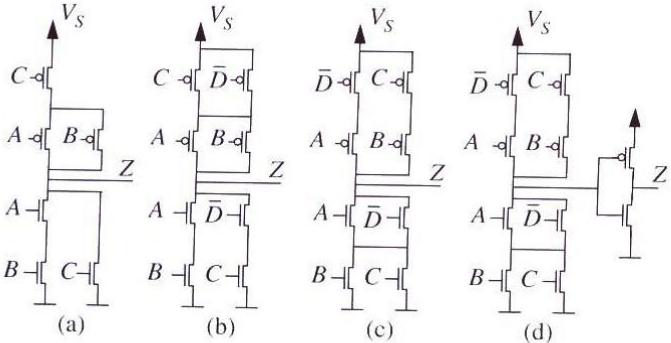


FIGURE 11.28