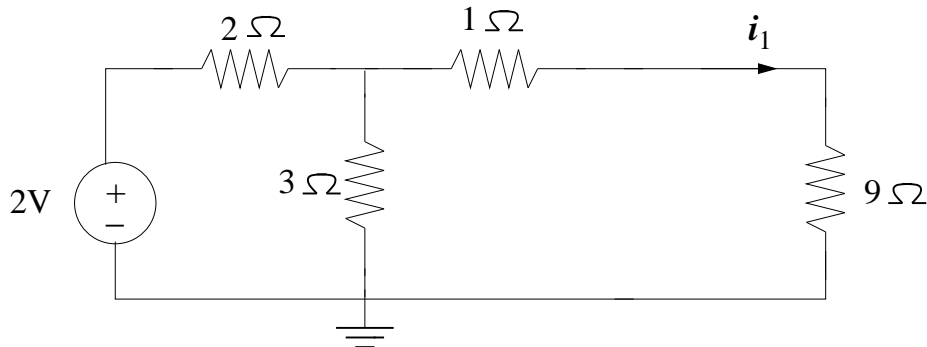


Problem 1: To find the current due to the 2V voltage source, we zero out the current source by making it an open circuit:



The resistance loading the voltage source is

$$R = 2 + \frac{3 \times 10}{3 + 10} = \frac{56}{13}$$


and so the source current is

$$i_s = \frac{2}{R} = \frac{26}{56}$$

By current division,

$$i_1 = \frac{i_s 3}{3 + 10} = \frac{6}{56} = \frac{3}{28} \approx 0.107$$

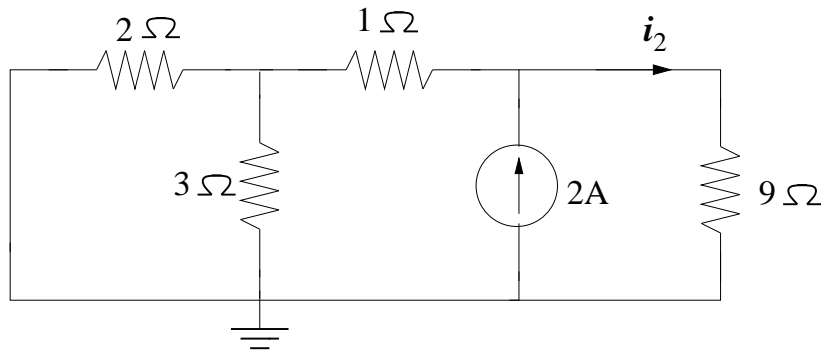To find the current due to the 2A current source, we zero out the voltage source by making it a short circuit:




To the left of the current source, 2 in parallel with 3 is $6/5$, and that's in series with 1, so that resistance is $11/5$. By current division,

$$i_2 = \frac{11/5}{11/5 + 9} \times 2 = \frac{11}{28} \approx 0.393$$

The total current is

$$i = i_1 + i_2 = \frac{3}{28} + \frac{11}{28} = \frac{14}{28} = 0.5$$

Problem 2: (8 points)

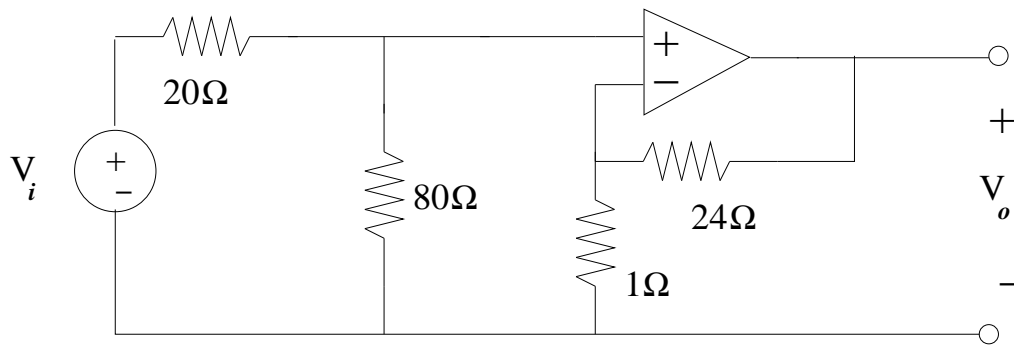

Using voltage division,

$$V_+ = V_i \frac{80}{20 + 80} = 0.8V_i$$

also


$$V_+ = V_- = V_o \frac{1}{1 + 24} = 0.04V_o$$

so


$$\frac{V_o}{V_i} = \frac{0.8}{0.04} = 20$$

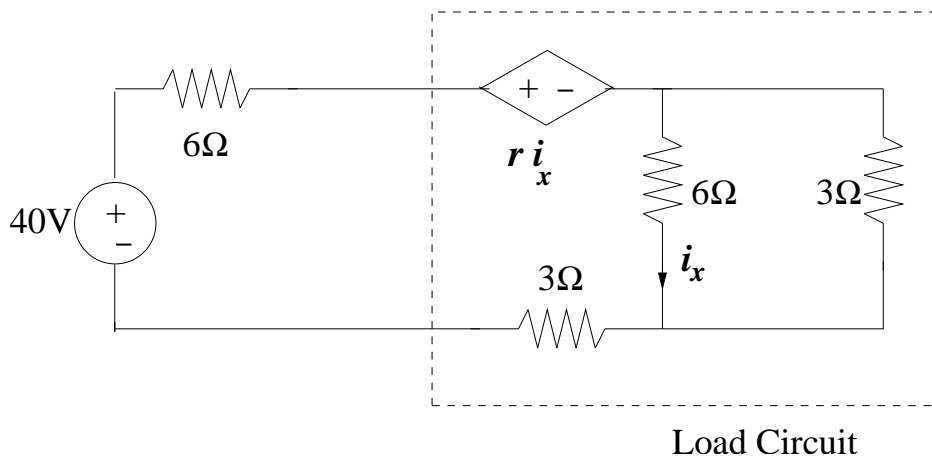Problem 3: (12 points)

In the following circuit, the value of r that will maximize the power delivered to the load circuit is when r is equal to the Thevenin equivalent resistance, which is 6Ω .



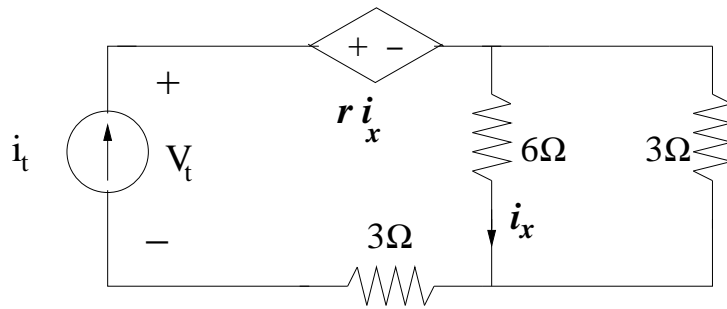The load circuit is equivalent to some resistor, since it has no independent sources. Let us find what resistance it is equivalent to by hooking it up to a test current source:



By current division,

$$i_x = \frac{i_t}{3}$$

Writing KVL around the left-hand loop and then substituting for i_x :

$$V_t = 3i_t + 6i_x + ri_x = 3i_t + \frac{6+r}{3}i_t$$

$$\frac{V_t}{i_t} = 3 + \frac{6+r}{3}$$

This needs to be equated to 6:


$$3 + \frac{6+r}{3} = 6 \rightarrow r = 3$$

Problem 4: (a) (2 points) Both Switches have been open for a very long time, and Switch 1 is closed at $t = 0$. When switch 1 is closed, the 30V source is directly across the 5Ω resistor. The node between switch 1 and switch 2 becomes part of the ground node. The right hand portion of the circuit is no longer connected to the source. So this is a natural response.

(b) (2 points) Switch 2 has been open for a very long time, and Switch 1 has been closed for a very long time, and then Switch 1 is opened at $t = 0$. When switch 1 is opened, the source is connected to the whole rest of the circuit, so this is a step response.

(c) (2 points) Both Switches have been open for a very long time, and Switch 2 is closed at $t = 0$. Also a step response, for the same reason as above.

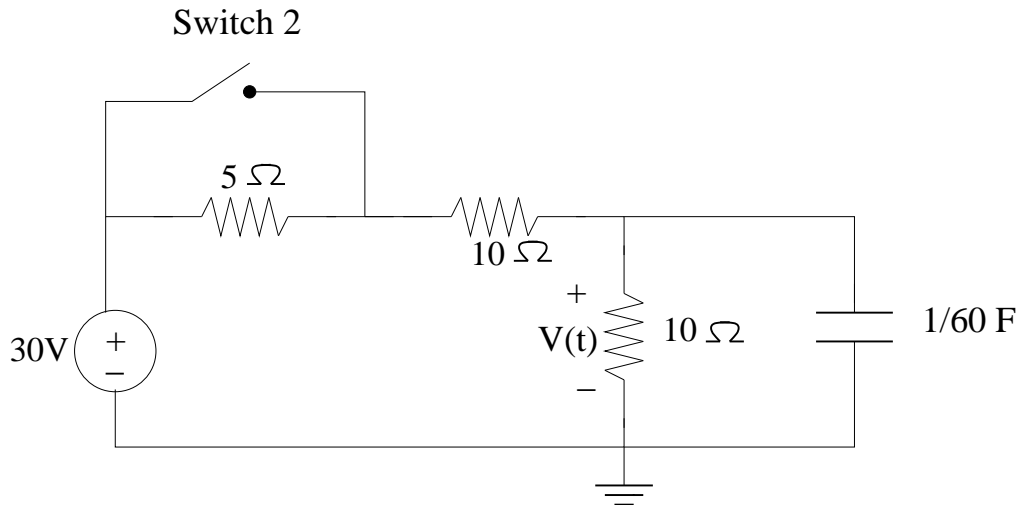(d) (8 points) Determine the voltage $V(t)$ for $t > 0$ for the circuit below, where Switch 2 has been closed for a very long time and opens at $t = 0$.



Before $t = 0$, the capacitor acts as an open circuit to DC, and the switch is closed. So the whole circuit just has a 30V source across two $10\ \Omega$ resistors. So $V(0^-) = 15V$.

Since the unknown voltage which we are trying to find is the voltage across a capacitor, the value at $t = 0^+$ is the same as the value at $t = 0^-$. For $t > 0$ we get by KCL:

$$\frac{1}{15}(v - 30) + \frac{1}{10}v + \frac{1}{60} \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} + 10v = 120$$

$$v = 12 + 3e^{-10t} \text{Volts}$$

Problem 5: (8 points) Since Z has a resistive component, one of the impedances must be a resistor. Let $Z_1 = R$. The other one must be a capacitor, since the imaginary portion of the impedance is negative. So $Z_2 = 1/j\omega C$. But if you don't see that the other component is a capacitor, you can always just try it both ways (inductor, capacitor) and see which one works.

The parallel combination of Z_1 and Z_2 has to be $5 - j5$

$$\frac{\frac{1}{j\omega C} R}{R + \frac{1}{j\omega C}} = 5 - j5$$

Multiplying the left hand side, top and bottom, by $j\omega C$ we get

$$\frac{R}{Rj\omega C + 1} = 5 - j5$$

$$R = 5Rj\omega C + 5 - j5 + 5R\omega C$$

which gives us two equations, one for the real part and one for the imaginary part:

$$5R\omega C - 5 = 0 \quad \text{and} \quad R = 5 + 5R\omega C$$


from which we get $R = 10\Omega$ and

$$C = \frac{1}{10\omega} = \frac{1}{102\pi 60} = 265\mu F$$

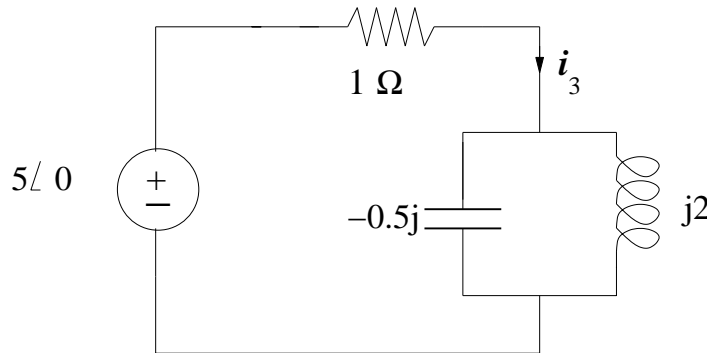Problem 6: (15 points) This problem must be solved by superposition. Keeping just the DC source, the circuit has only 1Ω resistor connected across a DC source, so $i_1 = -2.5A$.

Keeping the $\omega = 1$ source, the inductor behaves like $j\omega L = j$ and the capacitor behaves like $1/j\omega C = -j$. And, just like we did in class during the last lecture, an impedance of j in parallel with an impedance of $-j$ is infinite impedance, so the current is zero. $i_2 = 0$

Lastly, keeping the $\omega = 2$ source, the circuit becomes:



$$Z = 1 + (j2) \parallel (-j0.5) = 1.2\angle -33.7^\circ$$

$$I_3 = \frac{5}{1.2\angle -33.7^\circ} = 4.17\angle 33.7^\circ$$

So the final answer is the superposition:

$$i(t) = 4.17 \sin(2t + 37^\circ) - 2.5A$$

Problem 7: (6 points)

$$I_{eff} = \sqrt{\frac{1}{2} \int_0^1 2^2 dt + \int_1^2 (-1)^2 dt} = \sqrt{\frac{1}{2}(4 + 1)} = \sqrt{\frac{5}{2}} = 1.58$$

Problem 8: (15 points) (a) The voltage across the inductor is

$$V_L(t) = L \frac{di}{dt} = 10^{-2} \times \frac{0.1A}{10^{-3}s} = 1V$$

(b) Assuming no initial charge on the capacitor, its voltage is

$$V_C(t) = 0 + \frac{1}{10^{-5}} \int_0^t 100x dx = \frac{10^7}{2} t^2$$

(c) The stored energy in the capacitor is $\frac{1}{2}CV^2$ and the stored energy in the inductor is $\frac{1}{2}LI^2$. So

$$\frac{1}{2}10^{-5} \left(\frac{10^7 t^2}{2} \right)^2 > \frac{1}{2}10^{-2}(100t)^2 \rightarrow t > 0.632msec$$

Problem 9: (14 points) By KCL at the inverting input of the op amp

$$\frac{V_i}{R} + \frac{V_o}{R} + \frac{V_o}{1/j\omega C} = 0$$

This can be massaged around to give us:

$$H(j\omega) = \frac{V_o}{V_i} = \frac{-1}{1 + j\omega RC}$$

Thus we have

$$|H| = \frac{1}{\sqrt{(1 + (\omega RC)^2)}}$$

This is exactly the amplitude response of the first-order RC lowpass filter which we discussed in class, where it starts at 1 (for $\omega = 0$) and goes down to 0 (as $\omega \rightarrow \infty$) and passes through $1/\sqrt{2}$ at the half power frequency $\omega = 1/RC$.