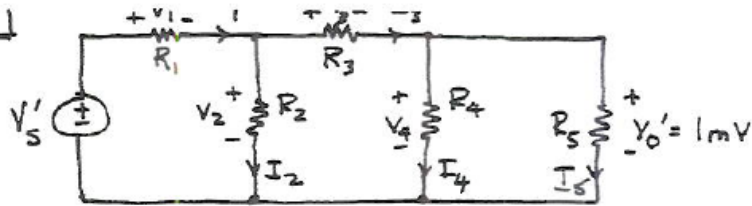


4.1

All $R = 2\text{ k}\Omega$ $V_s = 6\text{ V}$

$$I_5 = V_0'/R_5 = 1/2 \mu\text{A} \quad I_4 = V_0'/R_4 = 1/2 \mu\text{A} \quad I_3 = I_4 + I_5 = 1 \mu\text{A}$$


$$V_3 = I_3 R_3 = 2\text{ mV} \quad V_2 = V_3 + V_0' = 3\text{ mV} \quad I_2 = V_2/R_2 = 1.5 \mu\text{A}$$

$$I_1 = I_2 + I_3 = 2.5 \mu\text{A} \quad V_1 = I_1 R_1 = 5\text{ mV} \quad V_s' = V_1 + V_2 = 8\text{ mV}$$

$$\frac{V_0}{V_0'} = \frac{V_s}{V_s'} \Rightarrow V_0 = \left(\frac{6}{8\text{m}}\right)(1\text{m}) = 0.75\text{ V}$$

$$\boxed{V_0 = 0.75\text{ V}}$$

4.4

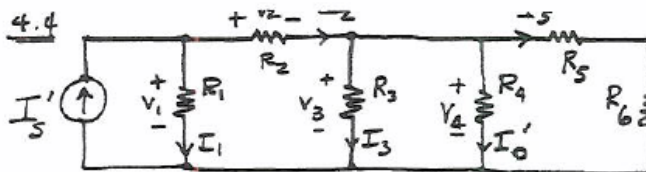 $R_4 = 4\text{ k}\Omega$ All other $R = 2\text{ k}\Omega$

$$I_s = 12\text{ mA} \quad I_0' = 1\text{ mA}$$

$$V_4 = I_0' R_4 = 4\text{ V} \quad I_5 = V_4/(R_5 + R_6) = 1\text{ mA}$$

$$V_3 = V_4 = 4\text{ V}$$

$$I_3 = V_3/R_3 = 2\text{ mA} \quad I_2 = I_3 + I_5 + I_0' = 4\text{ mA}$$

$$V_2 = I_2 R_2 = 8\text{ V}$$

$$V_1 = V_2 + V_3 = 12\text{ V}$$

$$I_1 = V_1/R_1 = 6\text{ mA}$$

$$I_s' = I_1 + I_2 = 10\text{ mA}$$

$$\frac{I_0}{I_0'} = \frac{I_s}{I_s'} \Rightarrow I_0 = \left(\frac{12\text{m}}{10\text{m}}\right)(1\text{m}) = 1.2\text{ mA}$$

$$\boxed{I_0 = 1.2\text{ mA}}$$