

Section 4.1

- 4.1 Find V_o in the network in Fig. P4.1 using linearity and the assumption that $V_o = 1$ mV.

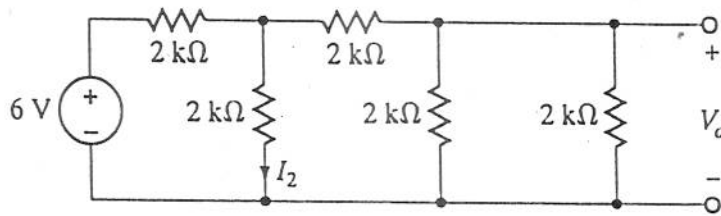


Figure P4.1

- 4.4 Find I_o in the network in Fig. P4.4 using linearity and the assumption that $I_o = 1$ mA.

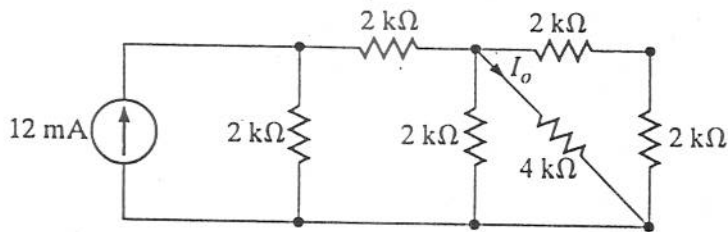


Figure P4.4