

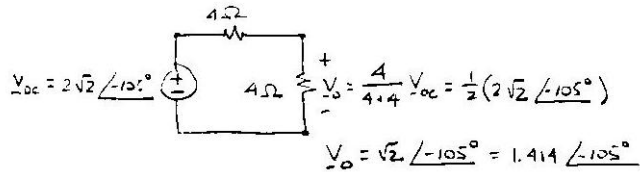

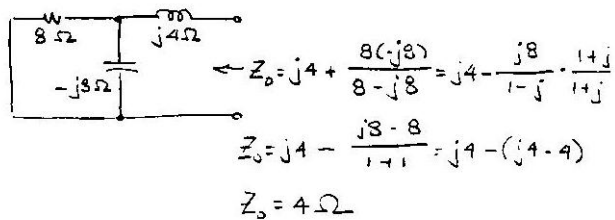
$$V_{oc} = \frac{-j}{1-j} (4 \angle 60^\circ) = \frac{1 \angle -90^\circ}{\sqrt{2} \angle -45^\circ} (4 \angle 60^\circ) = 2\sqrt{2} \angle -105^\circ$$


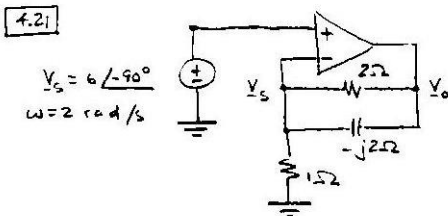
$$\therefore v_o(t) = \sqrt{2} \cos(2t - 105^\circ) = \underline{\underline{1.41 \cos(2t - 105^\circ) \text{ V}}}$$



By KCL at the inverting input of the op amp,

$$\frac{V_s}{1} + \frac{V_s - V_o}{2} + \frac{V_s - V_o}{-j2} = 0$$

$$V_s + \frac{1}{2} V_s - \frac{1}{2} V_o + j\frac{1}{2} V_s - j\frac{1}{2} V_o = 0$$

$$\left(\frac{3}{2} + j\frac{1}{2}\right) V_s = \left(\frac{1}{2} + j\frac{1}{2}\right) V_o$$


$$(3+j) V_s = (1+j) V_o$$

$$V_o = \frac{(3+j) V_s}{1+j} = \frac{(\sqrt{10} \angle 18.4^\circ)(6 \angle -90^\circ)}{\sqrt{2} \angle 45^\circ}$$

$$V_o = 6\sqrt{5} \angle -117^\circ = 13.4 \angle -117^\circ \text{ V}$$

$$\therefore v_o(t) = \underline{\underline{13.4 \cos(2t - 117^\circ) \text{ V}}}$$

4.22

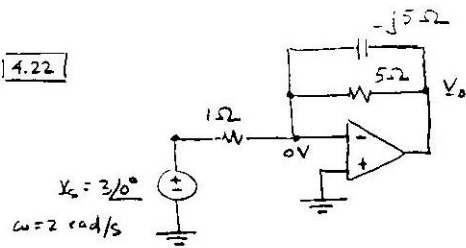

By KCL at the inverting input of the op amp,

$$\frac{v_s}{1} + \frac{v_o}{5} + \frac{v_o}{-j5} = 0$$


$$\frac{1}{5}(v_o + jv_o) = -v_s = -3\angle 0^\circ = 3\angle 180^\circ$$

$$\frac{1}{5}(1+j)v_o = 3\angle 180^\circ$$

$$v_o = \frac{5(3\angle 180^\circ)}{1+j} = \frac{15\angle 180^\circ}{\sqrt{2}\angle 45^\circ}$$


$$v_o = \frac{15}{\sqrt{2}}\angle 135^\circ = 10.6\angle 135^\circ$$
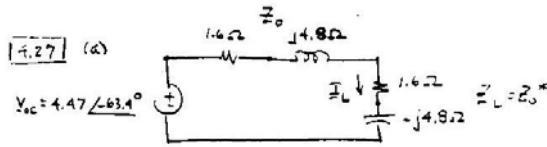
$$\therefore \underline{v_o(t) = 10.6 \cos(2t + 135^\circ) \text{ V}}$$



$$I_L = \frac{V_{oc}}{Z_0 + Z_L} = \frac{4.47 \angle -63.4^\circ}{3.2} = 1.40 \angle -63.4^\circ$$


$$\therefore P_L = \frac{1}{2} R_L |I_L|^2 = \frac{1}{2} (1.6) (1.4)^2 = \underline{1.57 \text{ W}}$$

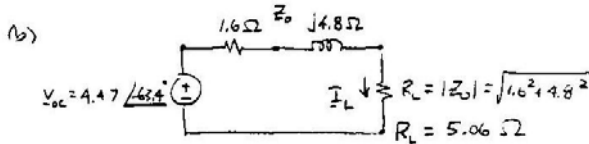

$$I_L = \frac{V_{oc}}{Z_0 + R_L} = \frac{4.47 \angle -63.4^\circ}{1.6 + j4.8 + 5.06} = \frac{4.47 \angle -63.4^\circ}{6.66 + j4.8}$$

$$I_L = \frac{4.47 \angle -63.4^\circ}{8.21 \angle 35.8^\circ} = 0.544 \angle -99.2^\circ \text{ A}$$

$$\therefore P_L = \frac{1}{2} R_L |I_L|^2 = \frac{1}{2} (5.06) (0.544)^2 = \underline{0.747 \text{ W}}$$

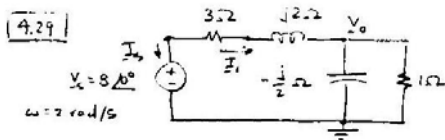

By KCL at node  $V_0$ ,

$$\frac{V_0 - 8}{3 + j2} + \frac{V_0}{-j2} + \frac{V_0}{1} = 0$$

$$\frac{V_0 - 8}{3 + j2} + j2V_0 + V_0 = 0$$

$$V_0 - 8 + (3 + j2)(j2V_0) + (3 + j2)V_0 = 0$$

$$V_0 - 8 - 4V_0 + j6V_0 + 3V_0 + j2V_0 = 0$$

$$j8V_0 = 8$$

$$V_0 = \frac{8}{j8} = -j1 = 1 \angle -90^\circ \Rightarrow I_1 = \frac{V_0 - V_0}{3 + j2} = \frac{8 + j}{3 + j2} = \frac{\sqrt{65} \angle 7.13^\circ}{\sqrt{13} \angle 32.7^\circ}$$

$$I_1 = \sqrt{5} \angle 26.6^\circ$$

$$I_2 = -I_1 = (-1)I_1 = (1 \angle 180^\circ)(\sqrt{5} \angle 26.6^\circ)$$

$$I_2 = \sqrt{5} \angle 153.4^\circ$$

For  $3\text{-}\Omega$  resistor,

$$P_3 = \frac{1}{2} R_3 |I_1|^2 = \frac{1}{2} (3) (\sqrt{5})^2 = \underline{7.5 \text{ W}}$$

For  $1\text{-}\Omega$  resistor,  $P_1 = \frac{1}{2} \frac{|V_0|^2}{R_1} = \frac{1}{2} \frac{(1)^2}{1} = \underline{0.5 \text{ W}}$

For inductor,  $P_L = \underline{0 \text{ W}}$

For capacitor,  $P_C = \underline{0 \text{ W}}$  } by inspection

For voltage source,

$$P_s = \frac{1}{2} |V_s| |I_1| \cos[\text{ang}(V_s) - \text{ang}(I_1)]$$

$$P_s = \frac{1}{2} (8) (\sqrt{5}) \cos(0^\circ + 153.4^\circ) = \underline{-8.0 \text{ W}}$$